

- Digital design ~~basic~~ (Review of concept)

Design specification:-

Digital Logic operations

NOT | AND | OR

Binary variable - {0, 1}

NOT

I/P	X	O/P	Y
	0		1
	1		0

$X \rightarrow Y$
 $Y = \bar{X}$

Boolean Expression

Truth table (one of the ways of specifying a design)

AND

I/P		O/P
X ₁	X ₂	Y
0	0	0
0	1	0
1	0	0
1	1	1

$Y = X_1 \cdot X_2 \rightarrow$ Boolean Exp.



Properties of AND gate.

- controlling input
- masking (AND)

OR

I/P		O/P
X ₁	X ₂	Y
0	0	0
0	1	1
1	0	1
1	1	1

$Y = X_1 + X_2 \rightarrow$ Boolean Exp.




Properties of OR gate

- controlling input
- masking (OR)

Universal gate:

NAND

IP		OP
x_1	x_2	Y
0	0	1
0	1	1
1	0	1
1	1	0

 


Implementation of other gate

- Inverter
- AND
- OR

De-morgan's law

NOR gate

IP		OP
x_1	x_2	Y
0	0	1
0	1	0
1	0	0
1	1	0

 

Implementation of other gate


- Inverter
- AND
- OR

By the use of De-morgan's law.

Derived gate:

XOR - (Exclusive OR)

x_1	x_2	Y
0	0	0
0	1	1
1	0	1
1	1	0

 


Properties of XOR gate

- Comparator / Equivalence checker
- Used as a buffer / inverter

- XOR -

x_1	x_2	y
0	0	1
0	1	0
1	0	0
1	1	1

$y = \overline{x_1 \oplus x_2}$

 

Large function (large no. of variables)

Three variable

$y = f(x_1, x_2, x_3)$

x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	
0	0	1	
1	1	1	

$k = 2^3$

- Ten variable -

$y = f(x_1, x_2, \dots, x_{10})$

Table size - 11 columns

- 2^{10} rows.

- n-variable

Table size = $(n+1)$ columns

- 2^n rows.

→ What is the total number of possible functions with n variables?

How to specify a complex design?

Example - Intel i-5 - its processor family was around 1000 - 2000 pins input/output

Use of programming language -

Hardware description language - (HDL)

Design specification

- Level of abstraction (Identifying the level of abstraction)
 - Architectural level
 - Behavior level
 - Structural level

- Design specification using language


- Architecture level languages
 - Blue spec
 - System C
 - System Verilog
 - (Use of python and other language)

~~RTL level~~
Behavioral level / Structural level

~~RTL Register Transfer level~~

- VHDL
- Verilog
- HDL (we will be coming in next class)

Modern Digital System Design Flow

 


Example

- ① Design of an auto pilot-micro controller
- Altitude
 - Temp
 - pressure
 - light
 - weather prediction

Design specification

 - ② Altitude - 30,000 ft
 Temp - 50°C to -10°C
 16 bit-Size pressure - ~~ft~~
 2mW power consumption
 Light -
 Weather - Rainy, cloud



④ VHDL, Verilog, HDL

```

module adder16 (input a16,
                input b16,
                output c16)
always @ (posedge clock)
begin
  c16 = a16 + b16
end
endmodule
  
```

```

input control = 2'b0001
begin
  c16 = a16 + b16
end
endmodule
  
```



5) Simulation to verify whether the design is correct or buggy

Test benches are used to supply input - and check the ~~design~~ desired output

6) Logic synthesis ..

this gives rise to gatelevel design (called gatelevel gate netlist)

